

Objectives

After completing this laboratory, a student will be able to:

1. determine the time constant of a RL circuit.
2. determine the inductance of an unknown inductor in an RL circuit
3. determine the resistance of an unknown resistor in an RL circuit

Procedure for Part 1: RC Circuit

1. Set up the circuit that is shown in Figure 3. Be sure that channel 1 and 2 are hooked up at the proper spots.

Exact setup procedure:

- From red FG plug CH1 red oscscope plug
- From black FG plug to CH1 black oscscope plug
- Also from red FG plug to leading side of Decade Resistance box (dial resistance to $< 100 \Omega$)
- Also from black side of FG plug to "E" plug on the 2.2 mH Inductor
- From trailing side of Decade Resistance box to "A" plug on 2.2 mH Inductor
- Also from "A" plug on Inductor to CH2 oscscope (single spring clamp hook from CH2)

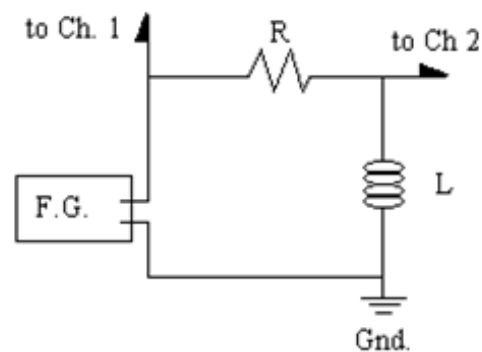


Figure 3

2. Set the FG to square wave and start in the vicinity of 1500Hz. With the oscscope Vert Mode set to CH1, select 1V/div for the vertical scale and use the Amplitude adjustment on the FG to fill the vertical scale of the oscscope screen (8V peak-to-peak). Set the horizontal time scale at 50 μ s/div.

3. Switch the oscilloscope to channel 2. Use the vertical and horizontal adjustment knobs to place the decay curve in a position which allows you to most easily locate the x/y intersection where τ is found. You may have to adjust the horizontal time scale and you may have to adjust the FG amplitude and frequency to get a nice looking decay curve on the oscscope screen.

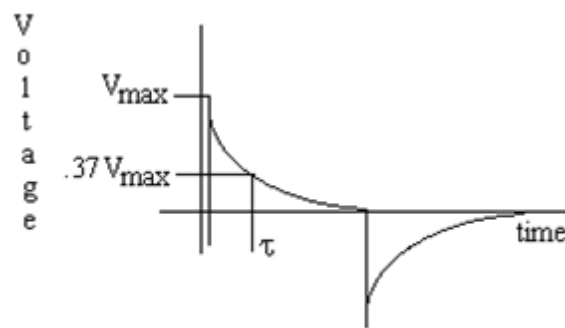


Figure 4

4. Measure τ from the oscilloscope screen, as shown in Figure 4, and record the value in the table on next page. This will be the **Observed** value for τ .
5. Unplug the plugs from the Decade Resistance box and measure the actual resistance using the multimeter (it should be very close to the dialed-in value). Record the actual resistance in the table.

6. Calculate the **Accepted** value for τ using your R and L values (you may assume the L value is as stated on the inductor). Record this value in the table.
7. Calculate the percent error between the experimental (**O**bserved) value and the calculated (**A**ccepted) value of τ using the formula $\%E_R = \frac{O-A}{A}(100)$. Record your % Error in the table.
8. Repeat steps 1 – 7 using the 36 mH inductor and a resistance value between 200 - 500 Ω
9. For Trial 3, you will determine the Inductance of the larger unknown inductor. You should dial the resistance to 15,000 – 18,000 Ω and make necessary adjustments on the oscscope to get a good looking decay curve. Using the τ from the oscscope and the known R, calculate L.
10. For Trial 4, you are to use your knowledge of what a good RL curve looks like on the oscilloscope and determine the inductance of the smaller unknown inductor. Dial in an appropriate resistance on the decade resistance box to establish a good RL curve.
11. For Trial 5, use the 2.2 mH inductor and the unknown (red dot) resistor. Adjust the settings on the oscscope to get a good looking decay curve, and determine the time constant from the decay curve, then use the time constant and the known L to calculate the **O**bserved R. Then, using the multimeter measure the **A**ccepted R and calculate the percent error.
12. For Trial 6, use the 36 mH inductor and the unknown (blue dot) resistor. Adjust the settings on the oscscope to get a good looking decay curve, and determine the time constant from the decay curve, then use the time constant and the known L to calculate the **O**bserved R. Then, using the multimeter measure the **A**ccepted R and calculate the percent error.

Trial	Inductance (mH)	Resistance (Ω)	Observed Time Constant from Oscscope (s)	Accepted Time Constant from Calculation (s)	% Error (%)
1	2.2				
2	36				
3				XXXXXXXXXX	XXXXXXXXXX
4				XXXXXXXXXX	XXXXXXXXXX
5	2.2			XXXXXXXXXX	
6	36			XXXXXXXXXX	